
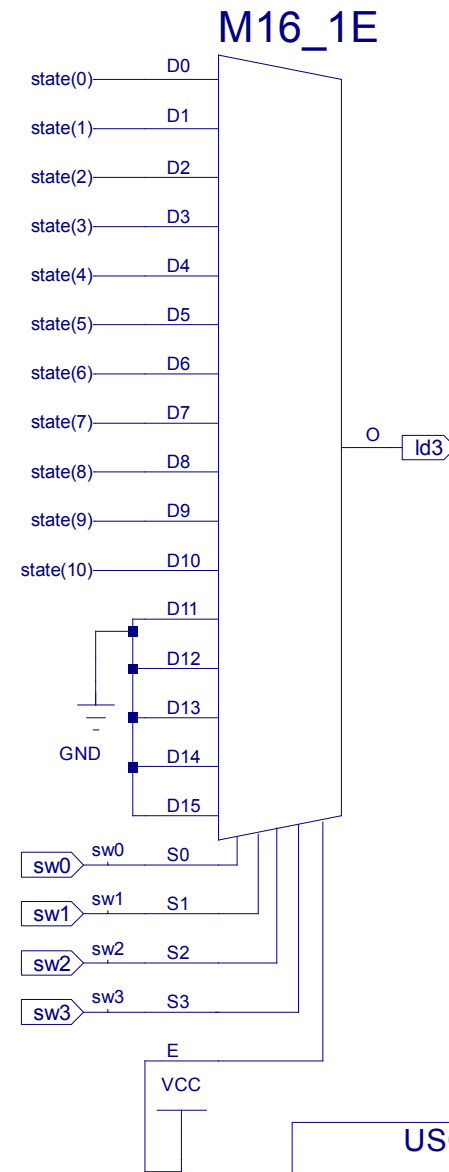



ee201l_number_lock

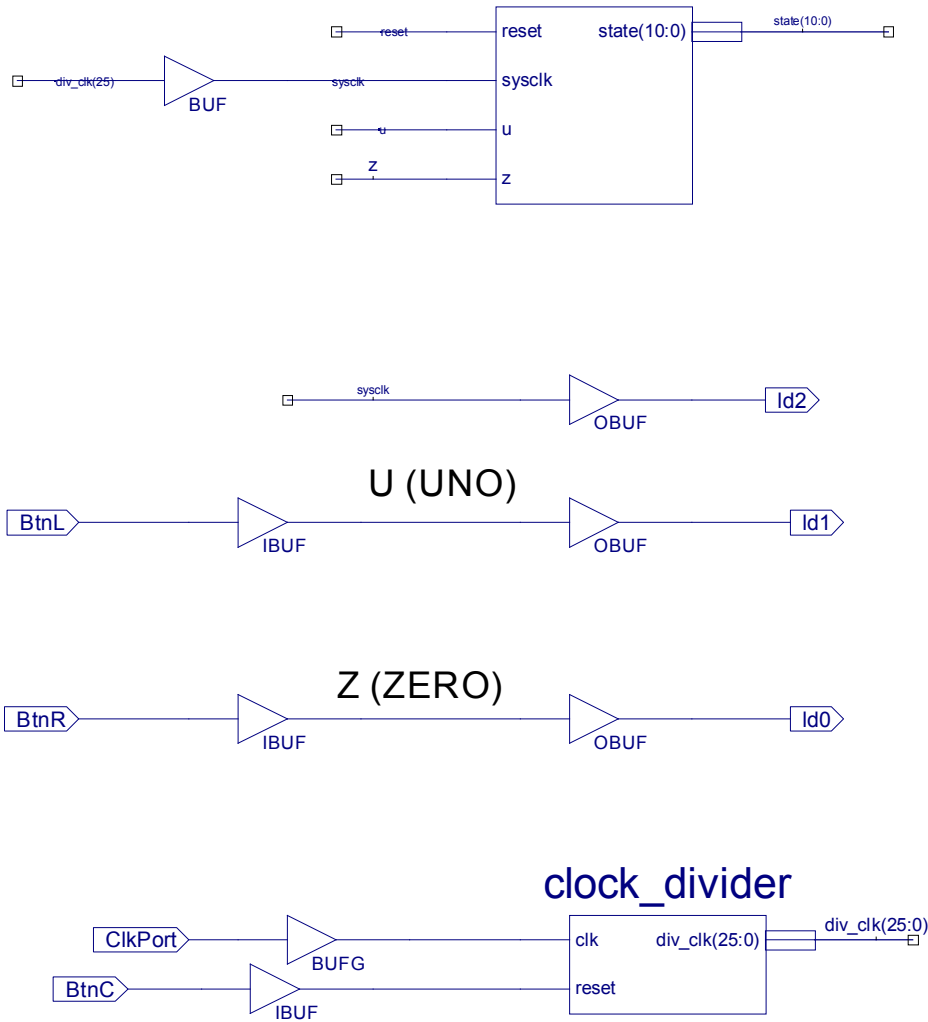

Sheet 1/3 Already complete!


USC VSoE CENG
EE201L Lab



Experiment:	Number Lock Top	Sheet	1/3
Designed by:	Gandhi Puvvada	Drawn by:	
Student:		Date	

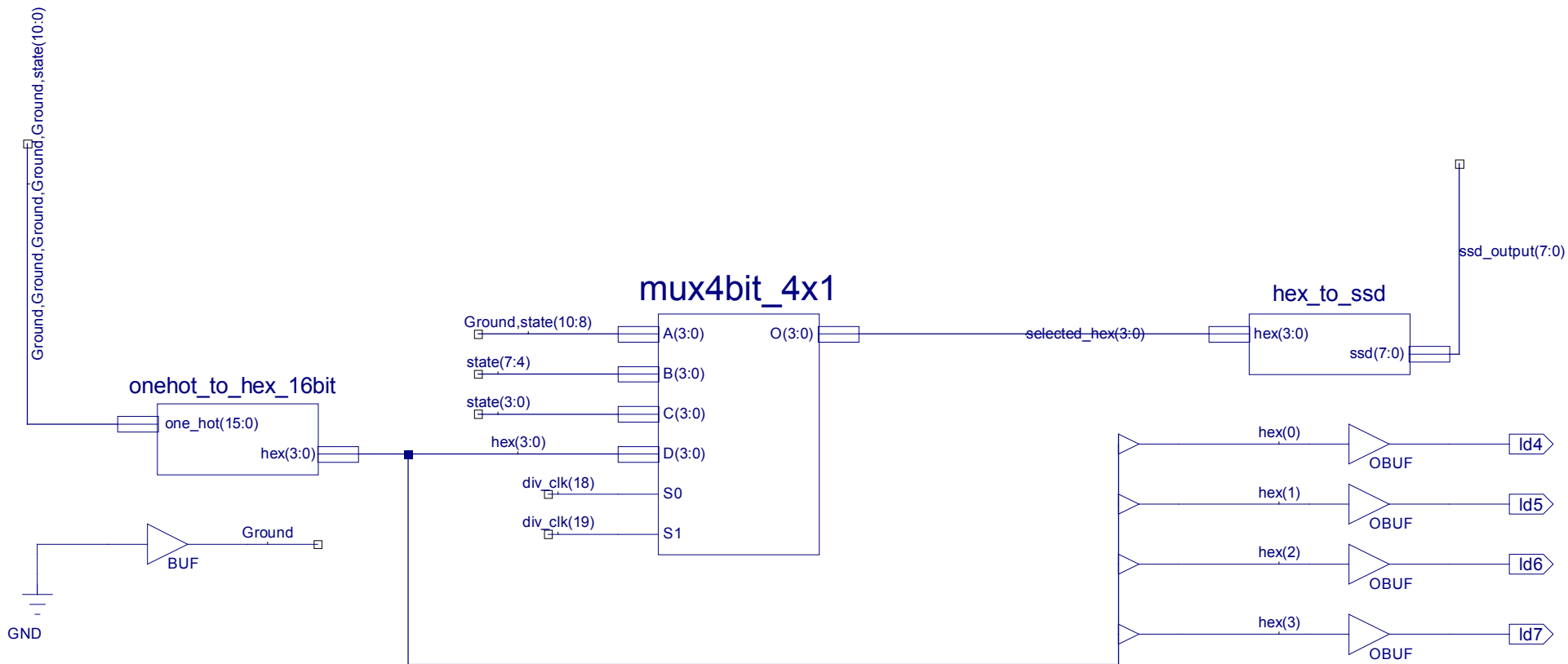

Sheet 2/3 To be completed by students

USC VSoE CENG	
EE201L Lab	
Experiment: Number Lock Top	Sheet 2/3
Designed by: Gandhi Puvvada	Drawn by: _____
Student: _____	Date: _____

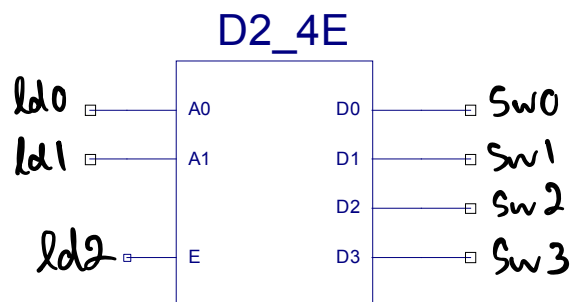

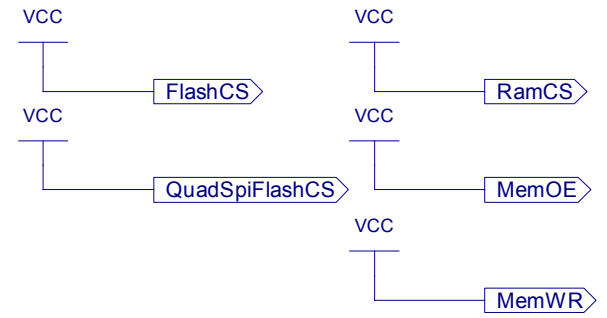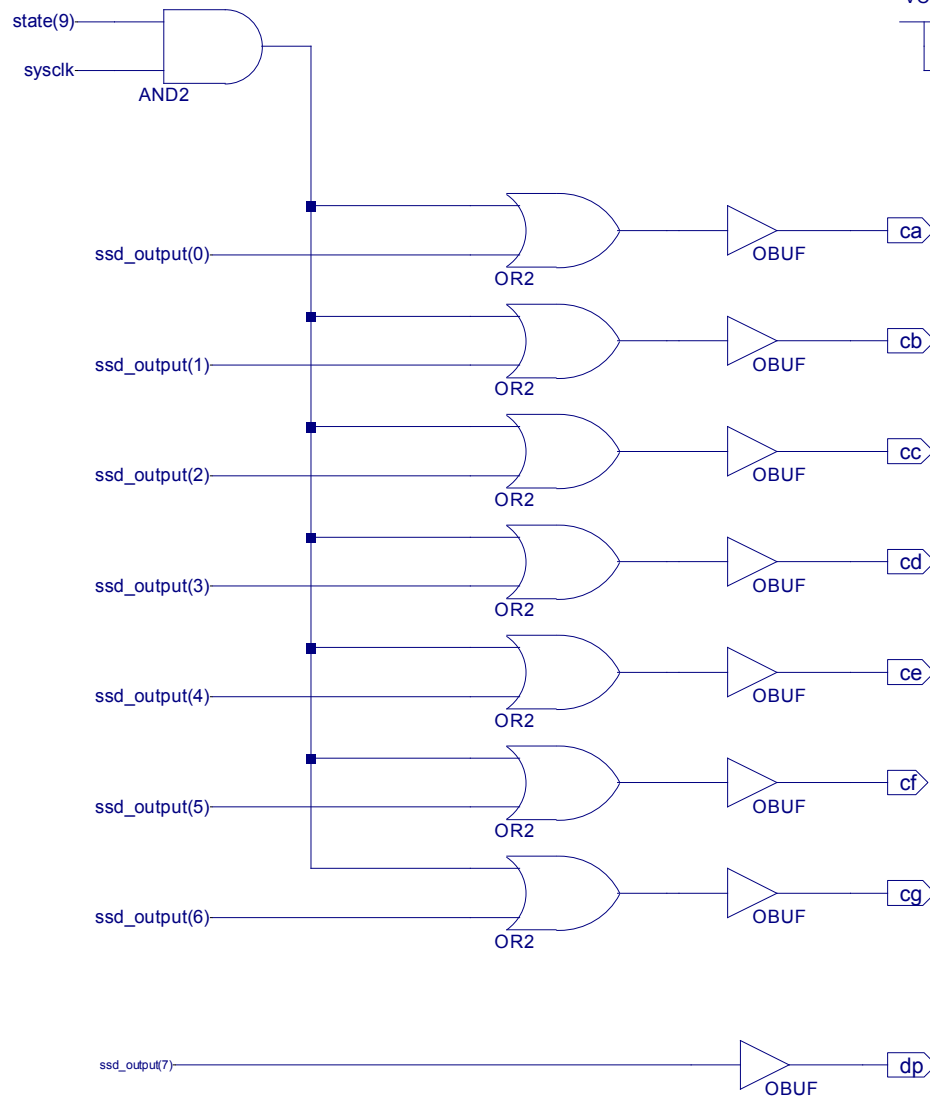

To disable the three memories

Sheet 3/3 Already complete!

USC VSoE CENG		
EE201L Lab		
Experiment:	Number Lock Top	Sheet 3/3
Designed by:	Gandhi Puwada	Drawn by:
Student:		